

FSPP0034 PHYSICS I

TUTORIAL 2

Chapter 2-4

1. To make a $0.40 \mu\text{F}$ capacitor, what area must the plates have if they are to be separated by a 2.8 mm air gap ?

[Ans: 130 m^2]

2. An electric field of $4.80 \times 10^5 \text{ V/m}$ is desired between two parallel plates, each of area 21.0 cm^2 and separated by 0.25 cm of air. What charge must be on each plate?

[Ans: $8.92 \times 10^{-9} \text{ C}$]

3. Suppose in Fig.1 that $C_1=C_2=C_3 = 16.0 \mu\text{F}$ and $C_4=28.5 \mu\text{F}$.

If the charge on C_2 is $12.4 \mu\text{C}$, determine :

(i) the charge on each of the capacitors

(ii) the voltage V_{ab}

[Ans: $Q_1=Q_2=12.4 \mu\text{C}$; $Q_3=24.8 \mu\text{C}$; $Q_4=37.2 \mu\text{C}$
 $V_1=V_2=0.775 \text{ V}$; $V_3= 1.55 \text{ V}$; $V_4=1.31 \text{ V}$; $V_{ab}=2.86 \text{ V}$]

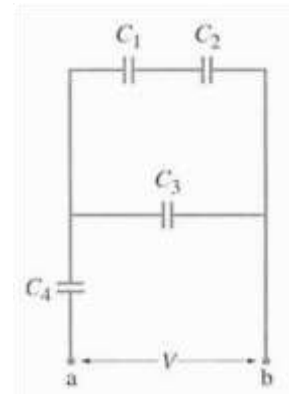


Figure 1

4. What is the capacitance of two square parallel plates 4.2 cm on a side that are separated by 1.8 mm of paraffin?

[Ans: $1.9 \times 10^{-11} \text{ F}$]

5. What is the diameter of a 1.00 m length of tungsten wire whose resistance is 0.32Ω ?

[Ans: $4.7 \times 10^{-4} \text{ m}$]

6. How much would you have to raise the temperature of copper wire (originally at 20°C) to increase its resistance by 15% ?

[Ans: 22°C]

7. A 115 V fish-tank heater is rated at 95 W . Calculate:

(a) the current through the heater when its operating

(b) its resistance

[Ans: (a) 0.83 A , (b) 140Ω]

8. An ac voltage, whose peak value is 180 V , is across a 380Ω resistor. What are the peak and rms currents in the resistor?

[Ans: (a) 0.33 A , (b) 0.47 A]

9. The peak value of an alternating current in a 1500 W device is 5.4 A . What is the rms voltage across it?

[Ans: 390 V]

10. A 0.65-mm -diameter copper wire carries a tiny current of $2.3 \mu\text{A}$. Estimate:

(a) the electron drift velocity, (b) the current density, and (c) the electric field in the wire.

[Ans: (a) $5.1 \times 10^{-10} \text{ ms}^{-1}$, (b) 6.9 Am^{-2} , (c) $1.2 \times 10^{-17} \text{ Vm}^{-1}$]

$$5) \rho = \frac{RA}{L}$$

$$5.6 \times 10^{-8} = \frac{0.32(\pi r^2)}{1}$$

$$r = 2.36 \times 10^{-4}$$

$$d = 2r = 4.72 \times 10^{-4} \text{ m}$$

$$6) \rho_T = \rho_0 (1 + \alpha(T - T_0)), \alpha = 0.0068$$

$$\text{let } \rho_0 = 1.68 \times 10^{-8}, \rho_T = 1.932 \times 10^{-8}$$

$$1.932 \times 10^{-8} = 1.68 \times 10^{-8} (1 + 0.0068(T - 20))$$

$$T = 42.06^\circ\text{C}, \Delta T = 42 - 20 = 22^\circ\text{C}$$

$$7) (a) \rho = VI$$

$$95 = 115(I)$$

$$I = 0.826 \text{ A}$$

$$(b) V = IR$$

$$115 = 0.826(R)$$

$$R = 139.21 \Omega$$

$$8) \rho = \frac{1}{2} I_0^2 R, \rho = \frac{1}{2} \frac{V_0^2}{R}$$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$

$$= 0.335 \text{ A}$$

$$\frac{180^2}{380} = I_0^2 (380)$$

$$I_0 = 0.474 \text{ A}$$

$$9) \rho = \frac{1}{2} I_0^2 R$$

$$1500 = \frac{1}{2} (5.4)^2 R$$

$$R = 102.88 \Omega$$

$$\rho = \frac{1}{2} \times \frac{V_0^2}{R}$$

$$1500 = \frac{1}{2} \times \frac{V_0^2}{102.88}$$

$$V_0 = 555.55 \text{ V}$$

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$$

$$= \frac{555.55}{\sqrt{2}}$$

$$= 392.84 \text{ V}$$

$$10) (a) v = \frac{I}{nAq}, n = 8.5 \times 10^{28} \text{ e}^-/\text{m}^3$$

$$= 2.3 \times 10^{-6}$$

$$\frac{8.5 \times 10^{28} (\pi \times 0.325^2) (1.6 \times 10^{-19})}{}$$

$$= 5.1 \times 10^{-10} \text{ ms}^{-1}$$

$$(b) \text{ current density} = \frac{\text{current}}{\text{area}} = \frac{2.3 \times 10^{-6}}{\pi \times 0.325 \times 10^{-3}^2} = 6.93 \text{ A m}^{-2}$$


1) $C = 0.40 \mu F$, $A = ?$, $d = 2.8 \text{ mm}$
 $C = \frac{\epsilon_0 A}{d}$, $0.40 \times 10^{-6} = \frac{8.85 \times 10^{-12} (A)}{2.8 \times 10^{-3}}$, $A = 126.55 \text{ m}^2$

2) $E = 4.80 \times 10^5$, $V = E d$, $A = \frac{21 \text{ cm}^2}{1} \times \frac{0.01}{1 \text{ cm}} \times \frac{0.01}{1 \text{ cm}} = 2.1 \times 10^{-3} \text{ m}^2$, $d = 2.5 \times 10^{-3} \text{ m}$

$$C = \frac{\epsilon_0 A}{d} = 7.434 \times 10^{-12} \text{ F}, \quad V = 4.80 \times 10^5 (2.5 \times 10^{-3}) = 1200 \text{ V}$$

$$Q = VC = 8.921 \times 10^{-9} \text{ C}$$

3)

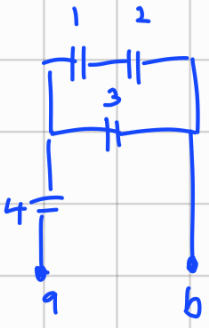

$\frac{1}{C_{12}} = \frac{1}{C_1} + \frac{1}{C_2}$
 $C_{12} = 8 \mu F$
 $C_{12} + C_3 = C_x$
 $C_x = 24 \mu F$
 $\frac{1}{C_y} = \frac{1}{C_x} + \frac{1}{C_4}$
 $C_y = 13.03 \mu F$

$Q_1 = Q_2 = Q_{12}$
 $= 12.4 \mu C$
 $Q_3 = V_3 C_3$
 $= 1.55 (16)$
 $= 24.8 \mu C$
 $Q_x = Q_4 = Q_{12} + Q_3$
 $= 12.4 + 24.8$
 $= 37.2 \mu C$

$$V_1 = V_2 = \frac{Q_1}{C_1}$$

$$= \frac{12.4}{16}$$

$$= 0.775 \text{ V}$$

$$V_3 = V_{12}$$

$$= 1.55 \text{ V}$$

$$V_4 = \frac{Q_4}{C_4}$$

$$= \frac{37.2}{28.5}$$

$$= 1.31 \text{ V}$$

$$V_{ab} = \frac{Q_x}{C}$$

$$= \frac{37.2}{13.03}$$

$$= 2.85 \text{ V}$$

$$V_{12} = 2(0.775)$$

$$= 1.55 \text{ V}$$

4) $A_{\text{req}} = 0.042 \times 0.042$
 $= 1.764 \times 10^{-3} \text{ m}^2$

$d = 1.8 \text{ mm}$
 $= 1.8 \times 10^{-3} \text{ m}$

$$C = \frac{A \epsilon_0}{d} = \frac{1.764 \times 10^{-3} \times 8.85 \times 10^{-12}}{1.8 \times 10^{-3}}$$

$$= 8.673 \times 10^{-12}$$

11. Calculate the terminal voltage for a battery with an internal resistance of $0.90\ \Omega$ and an emf of 6.00 V when the battery is connected in series with $81\ \Omega$ resistor.

[Ans: (a) 5.93 V]

12. Determine (a) the equivalent resistance of the circuit shown in Fig. 2,
(b) the voltage across each resistor,

[Ans: (a) $1332\ \Omega$, (b) $V_{960} = 8.6\text{ V}$, $V_{820} = V_{680} = 3.4\text{ V}$]

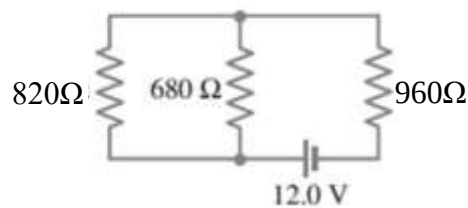


Figure 2

13. Calculate the currents in each resistor of Fig.3

[Ans: $I_{120} = I_{82} = 0.24\text{ A}$, $I_{64} = 0.15\text{ A}$, $I_{25} = I_{110} = 0.092\text{ A}$]

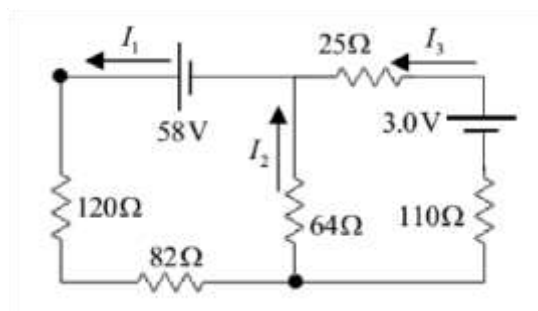


Figure 3

14. In Fig. 4 the total resistance is $15.0\text{ k}\Omega$ and the battery's emf is 24.0 V . If the time constant is measured to be $24.0\ \mu\text{s}$, calculate :

(a) the total capacitance of the circuit and

(b) the time it takes for the voltage across the resistor to reach 16.0 V after the switch is closed.

[Ans: (a) $C = 1.60 \times 10^{-9}\text{ F}$ (b) $t = 9.73\ \mu\text{s}$]

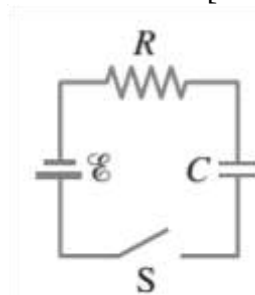


Figure 4

$$11) \quad \epsilon = I(R+r) \quad V = IR$$

$$6 = I(81+0.9) \quad = 0.073(81)$$

$$I = 0.073 \text{ A} \quad = 5.93 \text{ V}$$

$$12) (a) \quad R_1 = 820, R_2 = 680, R_3 = 960$$

$$\frac{1}{R_{12}} = \frac{1}{820} + \frac{1}{680}$$

$$= 371.73 \, \Omega$$

$$R_{\text{eff}} = R_{12} + R_3$$

$$= 371.73 + 960$$

$$= 1331.73 \, \Omega$$

$$(b) \quad V = IR \quad I = I_2 = I_3$$

$$12 = I(1332) \quad V_3 = 0.009(960)$$

$$I = 0.009 \text{ A} \quad = 8.64 \text{ V}$$

$$V_{12} = I_{12} R_{12} = V_1 = V_2 = 0.009(372)$$

$$= 3.348 \text{ V}$$

$$13) \quad I_1 = I_2 + I_3 \quad - (1)$$

$$58 = 202I_1 + 64I_2 \quad - (2)$$

$$3 = 135I_3 - 64I_2 \quad - (3)$$

$$61 = 202I_1 + 135I_3$$

$$61 = 202(I_2 + I_3) + 135I_3$$

$$61 = 202I_2 + 337I_3$$

$$3 = -64I_2 + 135I_3$$

$$183 = 606I_2 + 1011I_3$$

$$(-) \quad 183 = -3904I_2 + 8235I_3$$

$$0 = 4510I_2 - 7224I_3$$

$$4510I_2 = 7224I_3$$

$$I_2 = \frac{7224}{4510} I_3$$

$$3 = 135I_3 - 64\left(\frac{7224}{4510}\right)I_3$$

$$I_3 = \frac{3}{32.5}$$

$$= 0.092 \text{ A}$$

$$I_2 = \frac{7224 \times 0.092}{4510}$$

$$= 0.15 \text{ A}$$

$$I_1 = 0.242 \text{ A}$$

$$14) (a) \quad \tau = RC$$

$$C = \frac{Q}{V} = \frac{24 \times 10^{-6}}{15000}$$

$$= 1.6 \times 10^{-9} \text{ F}$$

$$(b) \quad V = V_0(1 - e^{-\frac{t}{RC}})$$

$$16 = 24 - 24e^{-\frac{t}{RC}}$$

$$-8 = -24e^{-\frac{t}{RC}}$$

$$\frac{1}{3} = e^{-\frac{t}{RC}}$$

$$\ln\left(\frac{1}{3}\right) = -\frac{t}{24 \mu\text{s}} \ln(e)$$